

SCHERING BRIDGE

(Model No : VSB - 07)



User Manual

Version 1.0

Technical Clarification /Suggestion :

 / 

Technical Support Division,


Vi Microsystems Pvt. Ltd.,

**Plot No :75, Electronics Estate,
Perungudi, Chennai - 600 096, INDIA.**

Ph: 91- 44-24961842, 91-44-24961852

Mail : service@vimicrosystems.com,

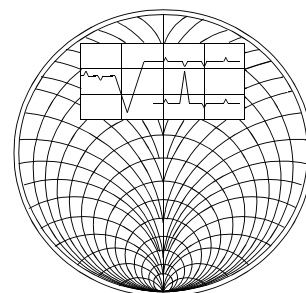Web : [www.vimicrosystem](http://www.vimicrosystem.com)





INTRODUCTION

Alternating current bridges are of outstanding importance for measurement of electrical quantities. Measurement of inductance, capacitance etc may be made conveniently and accurately by employing AC bridge networks. An AC bridge is an improved version of the wheatstone bridge and consists of a source of excitation and a detector sensitive to small alternating potential differences. The schering bridge is one such type of AC bridge used for the measurement of capacitances.

SCHERING BRIDGE

The schering bridge unlike the other bridges consists of four arms. One arm has a range selection is provided so as to select the correct point of balance of the bridge. This arm provides the point to select the range between which the bridge can be balanced. The other arm consists of a fixed capacitor connected in parallel to a variable resistance which is used as one of the variable arm of the bridge. The third arm has a standard variable resistance which is varied along with the other variable resistance to obtain exact balanced point. The circuit diagram and the phasor diagram of the bridge are as shown below,

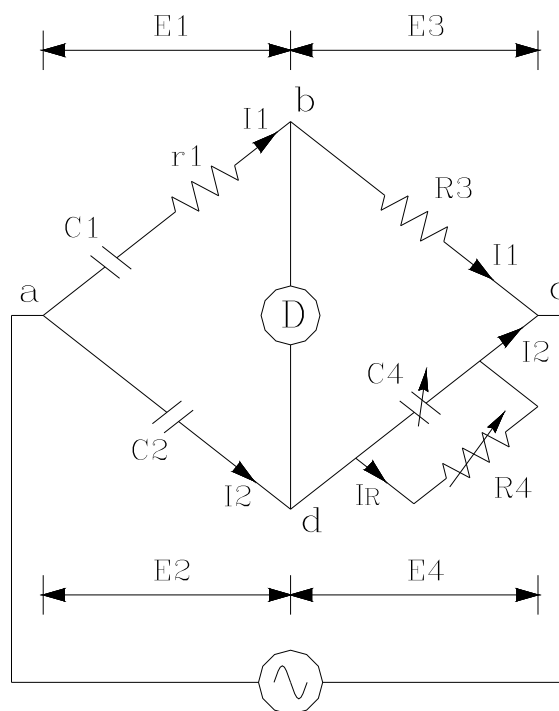

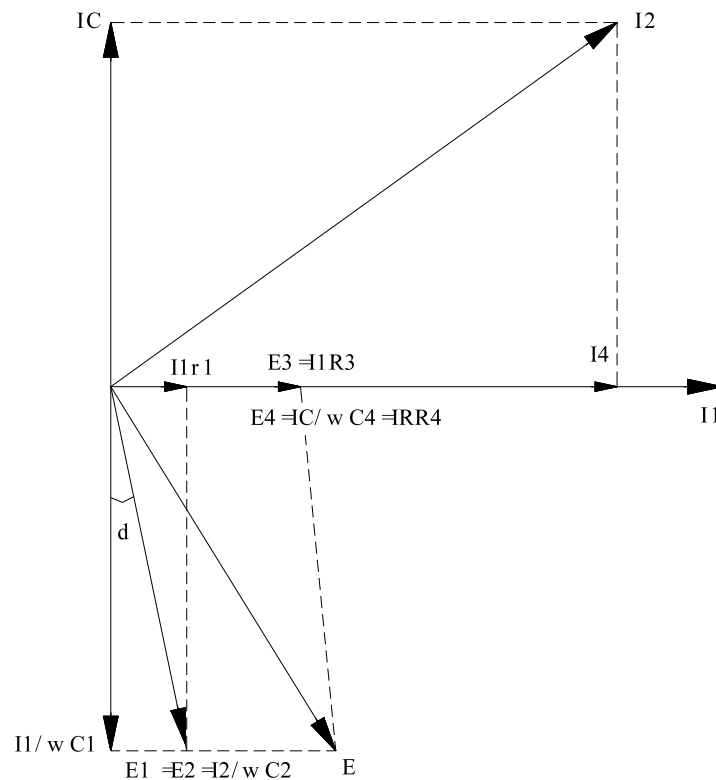

The balance condition for the bridge is as shown below

- Let
- C_1 = Capacitor whose capacitance is to be measured
 - r_1 = a series resistance representing the loss in the capacitor C_1
 - C_2 = a standard capacitor
 - R_3 = a non - inductive resistance
 - C_4 = a variable capacitor
 - R_4 = a variable non-inductive resistance in parallel with variable capacitor C_4

Therefore now at balanced condition,

$$\left[r_1 + \frac{1}{j\omega C_1} \right] \left[\frac{R_4}{1 + j\omega C_4 R_4} \right] = \frac{1}{j\omega C_2} \cdot R_3$$

$$\left[r_1 + \frac{1}{j\omega C_1} \right] R_4 = \frac{R_3}{j\omega C_2} (1 + j\omega C_4 R_4)$$

$$r_1 R_4 - \frac{jR_4}{\omega C_1} = - \frac{jR_3}{\omega C_2} + \frac{R_3 R_4 C_4}{C_2}$$

Equating real and imaginary terms, we get

$$r_1 = \frac{R_3 C_4}{C_2}$$

$$\text{and } C_1 = \frac{C_2 R_4}{R_3}$$

Two independent balance equations are obtained if C4 and R4 are chosen as the variable elements.

Dissipation factor

$$D_1 = \tan \delta = \omega C_1 r_1$$

$$= \omega \left(\frac{C_2 R_4}{R_3} \right) \times \left(\frac{R_3 C_4}{C_2} \right) = \omega C_4 R_4$$

Therefore values of capacitance C1 and its dissipation factor are obtained from the values of bridge elements at balance permanently setup schering bridges are sometimes arranged so that balancing is done by adjustment of R2 and C4 with C2 and R4 remaining fixed. Since R3 appears in both the balance equations and therefore there is some difficulty in obtaining balance but that will have same advantages as explained below.


The equation of the capacitance is

$$C_x = \left(\frac{R_4}{R_3} \right) C_2$$

and since R_4 & C_2 are fixed the dial resistor R_3 may be calibrated to read the capacitance directly. Dissipation factor $D_1 = \omega C_4 R_4$ and in case the frequency is fixed, the dial capacitor C_4 can be calibrated to read the dissipation factor directly. It should however be understood that the calibration for dissipation factor holds good for one particular frequency, but may be used at another frequency if correction is made by multiplying by the ratio of frequencies


The unit VSB - 07 has an inbuilt 1KHz oscillator circuit for giving input to the bridge and an audio amplifier with a speaker to detect the output. The speaker produces either no sound or least sound possible at the point of balance.

FRONT PANEL DIAGRAM

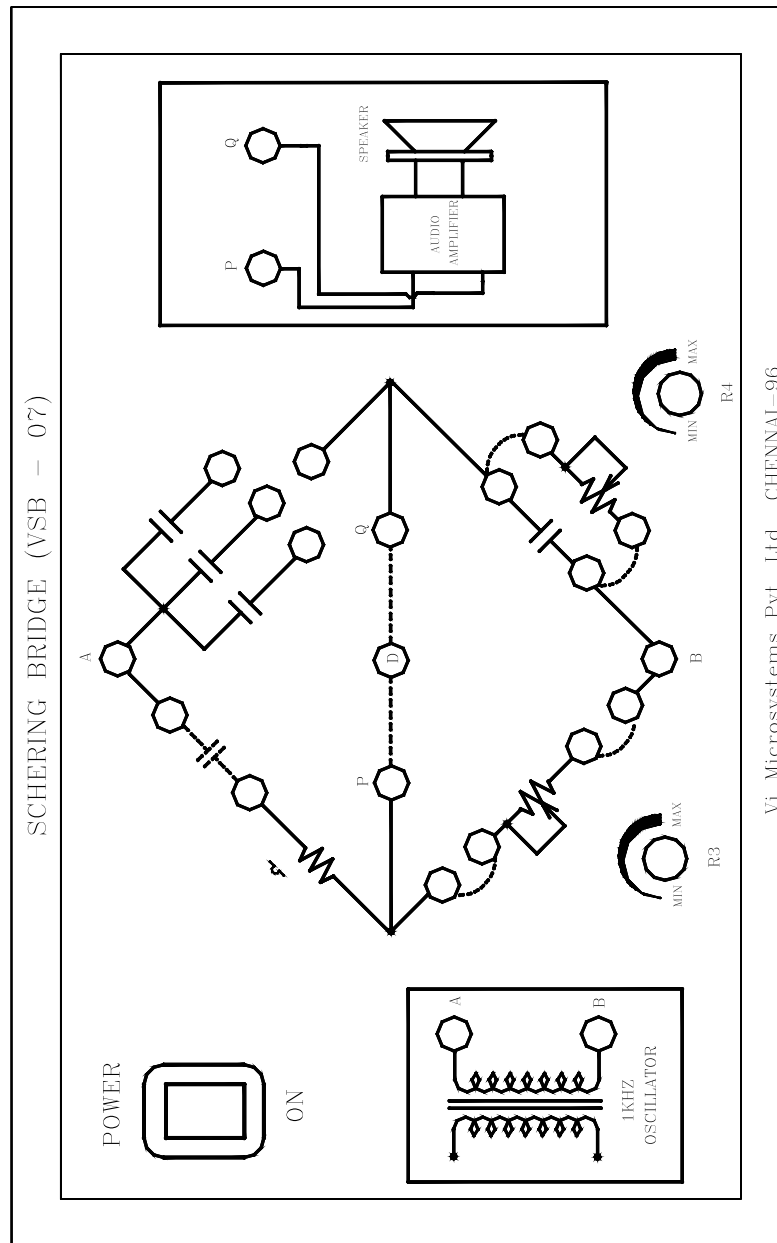

Vi Microsystems Pvt. Ltd., CHENNAI-96.

CONNECTION DIAGRAM

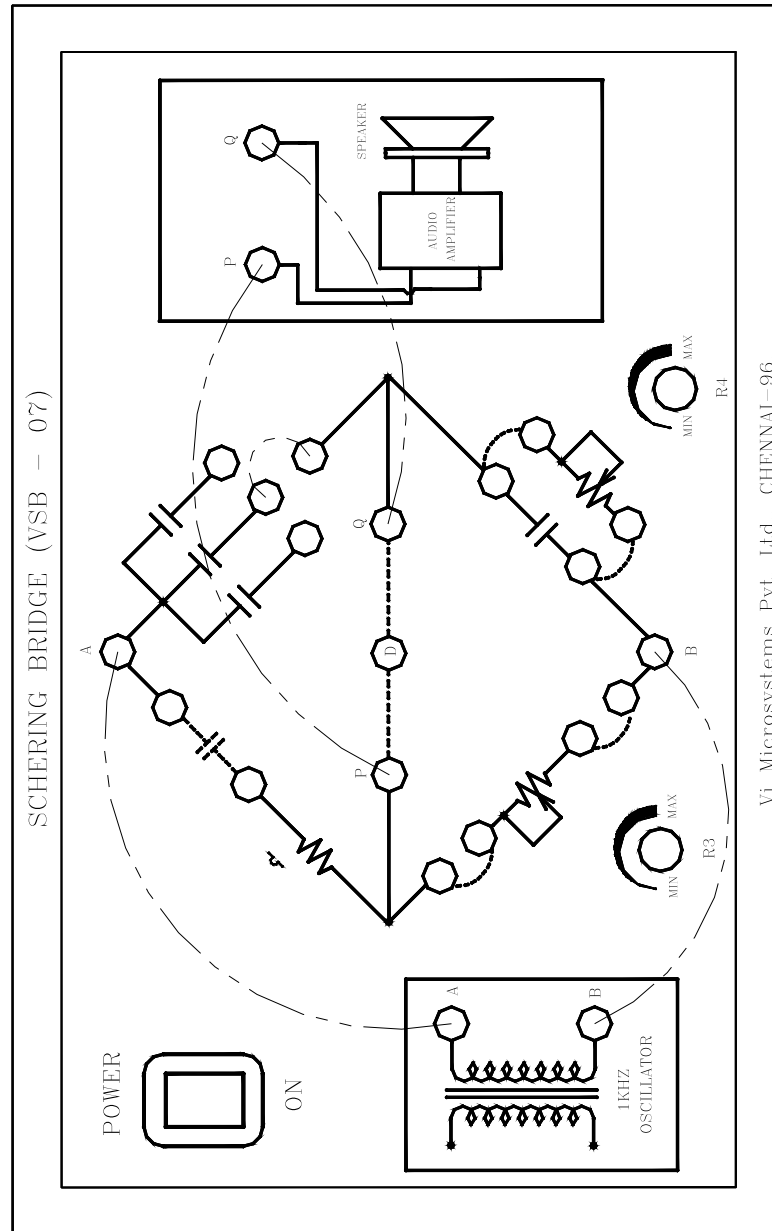

Vi Microsystems Pvt. Ltd., CHENNAI-96.

EXPERIMENT**AIM**

To find the value of unknown capacitance using a schering bridge.

REQUIREMENT

1. VSB - 07 Trainer Kit.
2. Decade Capacitance box.
3. Multimeter.
4. CRO.
5. Patch chords.

FORMULA USED

$$C_x = C_2 \left(\frac{R_4}{R_3} \right)$$

PROCEDURE - I

1. Connections are made as per the connection diagram shown above.
2. Connect the unknown capacitance at the Cx (unknown) point.
3. Keep R4, R3 in minimum position.
4. Connect the CRO across P and Q.
5. Switch ON the unit.
6. Vary resistance R3 to some extent. (above 2K is suggested).
7. Choose C2, such that you can obtain a maximum variation of output.

8. Vary the potentiometer R4 such that the amplitude of sine wave will decrease and at one point it will obtain a minimum of zero amplitude and then it will start increasing at that point stop the tuning and vary R3. Here also the amplitude of sine wave will decrease and at one point it will obtain a minimum of zero amplitude and then it will start increasing at that point stop the tuning.
9. Repeat the above step such that you will obtain minimum amplitude or zero amplitude.
10. Remove the patching at R4 and R3, find the resistance using multimeter and note down the reading according to the table given below and calculate the value of unknown capacitance.
11. One can verify the balancing condition by connecting the bridge output (P & Q) to the input (P & Q) of audio power amplifier and you can hear a minimum noise or no noise. If you vary the potentiometer R4 you can hear a maximum noise.

PROCEDURE - II

1. Connections are made as per the connection diagram shown above.
2. Connect the unknown capacitance at the Cx (unknown) point.
3. Keep R4, R3 in minimum position.
4. Connect the multimeter across P and Q (AC mode).
5. Switch ON the unit.
6. Vary resistance R3 to some extent. (above 2K is suggested).
7. Choose C2, such that you can obtain a maximum variation of output.
8. Vary the potentiometer R4 such that the output voltage will decrease and at one point it will obtain a minimum voltage or zero voltage and then it will start increasing at that point stop the tuning and vary R3. Here also the voltage will decrease and at one point it will obtain a minimum voltage or zero voltage and then it will start increasing at that point stop the tuning.
9. Repeat the above step such that you will obtain minimum voltage or zero voltage.
10. Remove the patching at R4 and R3, find the resistance using multimeter and note down the reading according to the table given below and calculate the value of unknown capacitance.
11. One can verify the balancing condition by connecting the bridge output (P & Q) to the input (P & Q) of audio power amplifier and you can hear a minimum noise or no noise. If you vary the potentiometer R4 you can hear a maximum noise.

TABULATION

S. No	C2 (μF)	R3 (Ohms)	R4 (Ohms)	Cx (Theoritical)	Cx (Practical)

RESULT

Thus the value of unknown capacitance was measured using a Schering Bridge.

CIRCUIT DIAGRAM:

